```
In [ ]: import numpy as np
        import pandas as pd
        import matplotlib.pyplot as plt
        import matplotlib.ticker as mtick
        from UliEngineering.EngineerIO import format_value
        from si_prefix import si_format
        import plecs_helper as helper
        %matplotlib
        %matplotlib inline
        # Imports and setup
        from pint import UnitRegistry
        from scipy.signal import find_peaks
        from scipy.optimize import fsolve
        # pandas display using scientific notation
        # pd.set_option('display.float_format', lambda x: f'{x:.3e}')
        # use pint
        units = UnitRegistry()
        units.default_format = "~P.2f"
        def to_decibels(arr, dc_gain = 0):
            return np.log10(np.abs(arr)) * 20 + dc_gain
```

Using matplotlib backend: TkAgg

Pre-Lab 11

We designed our compensator to have a gain crossover frequency at $\frac{1}{8}$ the switching frequency, or $\omega_{gc}=6.25kHz$. At this frequency, our plant has a gain of about $10dB\approx 3$, so we chose our overall gain to be $K_p=\frac{1}{3}$.

The phase margin of our plant (obtained in Lab 9) at the desired crossover frequency was very close to 90°, which would have left no phase margin once we added the integrator. Therefore, we relied on the lead element to generate the recommended phase margin of 60°---and what the heck, we went with 66°. I quite like this approach, as it gave us a large K value and a tall and wide phase boost. I do not see a downside to choosing an overly strong lead element, besides possibly the threat of overdamping.

We used the equations for the compensator components derived at the end of Lesson 13. The first time we calculated these values in class, we had an error of 2π because we did not convert the crossover frequency from revolutions per second (Hertz) to radians per second for ω_c . We re-calculated the values and used the highlighted row below.


```
In [ ]: def find_values(Rf1_unitless):
    Vout = 10 * units.volt
    Rf1 = Rf1_unitless * units.ohm
    Rf2 = Rf1 / 3 # 3 to 1 voltage divider produces 2.5V given a 10V input
```

```
wc = 50 * units.kilohertz * units.revolutions / 8
    angle boost = 66 * units.degree
    K = np.tan((angle_boost / 2 + 45 * units.degree))
    Kp = 1 / 3
    WZ = WC / K
    wp = wc * K
    Gc0 = Kp * wc * np.sqrt((1 + K ** (-2)) / (1 + K ** 2))
    Cc1 = 1 / (Gc0 * Rf1)
    Rc1 = 1 / (wz * Cc1)
    Cc2 = 1 / (wp * Rc1)
    print(f"K: {K},\t Gc0: {Gc0.to_compact()},\t Rf1: {Rf1.to_compact(units.ohm)},\
for R in [2, 2.2, 2.7, 3.3, 3.9, 4.3, 4.7, 5.1, 5.6, 6.2, 6.8, 7.5, 8.2, 10]: # val
    if R == 7.5:
        print() # highlight the chosen value
    find_values(R * 1e3)
    if R == 7.5:
        print()
K: 4.70,
                 Gc0: 442.83 Hz·turn,
                                           Rf1: 2.00 k\Omega,
                                                            Rf2: 666.67 Ω,
                                                                             Rc1: 666.
        Cc1: 179.70 nF,
67 Ω,
                                  Cc2: 8.12 nF
K: 4.70,
                 Gc0: 442.83 Hz·turn,
                                           Rf1: 2.20 k\Omega,
                                                            Rf2: 733.33 \Omega, Rc1: 733.
         Cc1: 163.37 nF,
                                 Cc2: 7.38 nF
33 Ω,
                 Gc0: 442.83 Hz·turn,
                                           Rf1: 2.70 k\Omega,
                                                            Rf2: 900.00 \Omega, Rc1: 900.
K: 4.70,
00 Ω,
         Cc1: 133.11 nF,
                                  Cc2: 6.01 nF
K: 4.70,
                 Gc0: 442.83 Hz·turn,
                                           Rf1: 3.30 k\Omega,
                                                            Rf2: 1.10 k\Omega,
                                                                             Rc1: 1.10
kΩ,
         Cc1: 108.91 nF,
                                  Cc2: 4.92 nF
                 Gc0: 442.83 Hz·turn,
                                                            Rf2: 1.30 k\Omega,
                                                                             Rc1: 1.30
K: 4.70,
                                         Rf1: 3.90 kΩ,
                                  Cc2: 4.16 nF
         Cc1: 92.16 nF,
K: 4.70,
                 Gc0: 442.83 Hz·turn,
                                                            Rf2: 1.43 k\Omega,
                                                                             Rc1: 1.43
                                           Rf1: 4.30 k\Omega,
                                  Cc2: 3.78 nF
kΩ,
         Cc1: 83.58 nF,
K: 4.70,
                 Gc0: 442.83 Hz·turn,
                                           Rf1: 4.70 kΩ,
                                                            Rf2: 1.57 k\Omega,
                                                                             Rc1: 1.57
                                  Cc2: 3.45 nF
         Cc1: 76.47 nF,
kΩ,
K: 4.70,
                 Gc0: 442.83 Hz∙turn,
                                          Rf1: 5.10 k\Omega,
                                                            Rf2: 1.70 k\Omega,
                                                                             Rc1: 1.70
kΩ,
         Cc1: 70.47 nF,
                                  Cc2: 3.18 nF
K: 4.70,
                 Gc0: 442.83 Hz·turn,
                                           Rf1: 5.60 k\Omega,
                                                            Rf2: 1.87 k\Omega,
                                                                             Rc1: 1.87
         Cc1: 64.18 nF,
                                  Cc2: 2.90 nF
                                                            Rf2: 2.07 k\Omega,
                                                                             Rc1: 2.07
K: 4.70,
                 Gc0: 442.83 Hz·turn,
                                         Rf1: 6.20 k\Omega,
                                  Cc2: 2.62 nF
         Cc1: 57.97 nF,
                 Gc0: 442.83 Hz·turn,
                                          Rf1: 6.80 k\Omega,
                                                            Rf2: 2.27 k\Omega,
                                                                             Rc1: 2.27
K: 4.70,
                                  Cc2: 2.39 nF
kΩ,
         Cc1: 52.85 nF,
                Gc0: 442.83 Hz·turn,
K: 4.70,
                                          Rf1: 7.50 k\Omega,
                                                            Rf2: 2.50 k\Omega,
                                                                             Rc1: 2.50
        Cc1: 47.92 nF,
                                 Cc2: 2.17 nF
K: 4.70,
                 Gc0: 442.83 Hz·turn,
                                           Rf1: 8.20 k\Omega,
                                                            Rf2: 2.73 k\Omega,
                                                                             Rc1: 2.73
         Cc1: 43.83 nF,
                                 Cc2: 1.98 nF
                                           Rf1: 10.00 kΩ, Rf2: 3.33 kΩ,
K: 4.70,
                  Gc0: 442.83 Hz·turn,
                                                                             Rc1: 3.33
                                Cc2: 1.62 nF
         Cc1: 35.94 nF,
```

Lab 11

Ian Eykamp

 The components we used were Rf1 = 7.50 kOhm, Rf2 = 2.49 kOhm, R5 = 2.49 kOhm



The impedance value as a function of frequency (as well as much of the analysis) is analyzed similarly to in Lab 10. I will skip most of the derivations and focus on comparing the behavior of the new and old compensators.


Compared with the Lab 10 compensator, the current design has a lower cross-over frequency, larger K value, and larger phase boost due to the lead element. This is desirable, because it increases our phase margin significantly while not affecting the integrator component at low frequencies.

```
In [ ]: R2 = 7.5e3 # * units.kiloohm
R3 = 2.49e3 # * units.kiloohm
Vtarget = 2.5 * (R2 + R3) / R3 # * units.volt
print(f"The expected output voltage given the voltage divider resistors is: {si_for
C1 = 47e-9 # * units.nanofarad
```


```
C2 = 2.2e-9 # * units.nanofarad
R5 = 2.49e3 # * units.ohm
w = np.logspace(1, 7, 100) # * units.hertz
def get_Zc(my_w):
   my_Zc = 1 / (1 / (R5 + 1 / (2 * np.pi * 1j * my_w * C1)) + 1 / (1 / (2 * np.pi
   return my_Zc
Zc = get_Zc(w) # direct equation
def get_Zc_lab10(my_w_lab10):
   my_{Zc} = (2 * np.pi * 1j * w / (40e3) + 1) / ((2 * np.pi * 1j * w / (1.9e7))
   return my_Zc_lab10
Zc_lab10 = get_Zc_lab10(w)
expected_wc = 1 / (R5 * np.sqrt(C1 * C2)) / 2 / np.pi # to get it into Hz
print(f"Lead\ element\ center\ voltage\ (\omega_c): \{si\_format(expected\_wc,\ precision\ =\ 2)\}H
fig, (ax1, ax2) = plt.subplots(nrows = 2, ncols = 1, sharex = False, sharey = False
helper.axes_labels("", "Hz", "Gain", "dB", title = "Zc Gain vs. Frequency (Magnitud
ax1.semilogx(w, to_decibels(Zc), linestyle = "solid", label = "Zc Magnitude (direct
ax1.semilogx(w, to_decibels(Zc_lab10), linestyle = "dashed", color = "purple", labe
ax1.axvline(x = expected_wc, linestyle = "dashed", color = "red", label = "Expected
ax1.axvline(x = 50e3, linestyle = "dashed", color = "black", label = "Switching Fre
ax1.legend(loc = "lower left")
helper.axes_labels("Frequency (Hz)", "Hz", "Impedance Angle (degrees)", "o", title
ax2.semilogx(w, np.angle(Zc, deg = True), linestyle = "solid", label = "Zc Angle")
ax2.semilogx(w, np.angle(Zc_lab10, deg = True), linestyle = "dashed", color = "purp
ax2.axvline(x = expected_wc, linestyle = "dashed", color = "red", label = "Expected
ax2.axvline(x = 50e3, linestyle = "dashed", color = "black", label = "Switching Fre
ax2.legend(loc = "upper left")
# ax2.set_ylim(-100, -80)
```

The expected output voltage given the voltage divider resistors is: 10.03 V Lead element center voltage (ω_c): 6.29 kHz

 Out[]: <matplotlib.legend.Legend at 0x190eb6f1880>



Bode Plots

 


Open-Loop Transfer Function (GOL)

```
In [ ]: w = open_loop_bode["Frequency (Hz)"]
        Zc = get_Zc(w)
        dc_gain = 18.58 \# dB
        G = 1 / ((w * 1j / 2.4e3) + 1) / ((w * 1j / 2.4e4) + 1) * 10**(dc_gain / 20) # opti
        open_loop_gc = open_loop_bode[(open_loop_bode["Channel 2 Magnitude (dB)"] < 0) & (o</pre>
        open_loop_gc_freq = open_loop_gc["Frequency (Hz)"]
        open_loop_gc_phase_margin = 180 - np.abs(open_loop_gc["Channel 2 Phase (deg)"])
        print(f"Open-loop gain cross-over frequency: {si_format(open_loop_gc_freq, precision)
        print(f"Open-loop gain cross-over phase margin: {np.round(open_loop_gc_phase margin
        open_loop_pc = open_loop_bode[(open_loop_bode["Channel 2 Phase (deg)"] < -180)].ilo</pre>
        open_loop_pc_freq = open_loop_pc["Frequency (Hz)"]
        open_loop_pc_gain_margin = open_loop_pc["Channel 2 Magnitude (dB)"]
        print(f"Open-loop phase cross-over frequency: {si_format(open_loop_pc_freq, precisi
        print(f"Open-loop phase cross-over gain margin: {np.round(open_loop_pc_gain_margin,
        fig, (ax1, ax2) = plt.subplots(nrows = 2, ncols = 1, sharex = False, sharey = False
        helper.axes_labels("", "Hz", "Gain (dB)", "dB", title = "Bode Plot for Open Loop Tr
```

```
ax1.semilogx(open_loop_bode["Frequency (Hz)"], open_loop_bode["Channel 2 Magnitude
ax1.semilogx(open_loop_lab10["Frequency (Hz)"], open_loop_lab10["Channel 2 Magnitud
# ax1.semilogx(open_loop_bode["Frequency (Hz)"], to_decibels(Zc), linestyle = "dash
# ax1.semilogx(open_loop_bode["Frequency (Hz)"], to_decibels(G), linestyle = "dashe
ax1.semilogx(open_loop_bode["Frequency (Hz)"], to_decibels(G * Zc), linestyle = "da
ax1.axhline(y = 0, color = "black", linestyle = "dashdot", linewidth = 0.5, alpha =
ax1.semilogx(open_loop_gc_freq, 0, marker = 's', markersize = 6, markerfacecolor =
ax1.semilogx([open_loop_pc_freq, open_loop_pc_freq], [0, open_loop_pc_gain_margin],
ax1.legend(loc = "lower left")
helper.axes_labels("Frequency (Hz)", "Hz", "Angle (degrees)", "o", title = "Bode Pl
ax2.semilogx(open_loop_bode["Frequency (Hz)"], np.unwrap(open_loop_bode["Channel 2
ax2.semilogx(open_loop_lab10["Frequency (Hz)"], np.unwrap(open_loop_lab10["Channel
# ax2.semilogx(open_loop_bode["Frequency (Hz)"], np.unwrap(np.angle(Zc, deg = True)
# ax2.semilogx(open_loop_bode["Frequency (Hz)"], np.unwrap(np.angle(G, deg = True),
ax2.semilogx(open_loop_bode["Frequency (Hz)"], np.unwrap(np.angle(G * Zc, deg = Tru
ax2.axhline(y = -180, color = "black", linestyle = "dashdot", linewidth = 0.5, alph
ax2.semilogx([open_loop_gc_freq, open_loop_gc_freq], [-180, -180 + open_loop_gc_pha
ax2.semilogx(open_loop_pc_freq, -180, marker = 's', markersize = 6, markerfacecolor
ax2.legend(loc = "lower left")
```

```
Open-loop gain cross-over frequency: 6.04 kHz
Open-loop gain cross-over phase margin: 68.84°
Open-loop phase cross-over frequency: 20.10 kHz
Open-loop phase cross-over gain margin: -9.99dB
```

 Out[]: <matplotlib.legend.Legend at 0x190e46da610>




This bode plot was taken on the upstream (closer to Vout) side of the feedback loop with reference to the downstream (closer to VFB) side of the injected current. Thus, the response of the system in this configuration corresponds with the **open-loop** transfer function G_{OL} , since the feedback loop is **factored out**.

As in Lab 10, the open-loop transfer function matches well with the theoretical curve until slightly past the gain crossover frequency. After this point, the experimental gain is larger and the angle is more negative than the theoretical. The theotetical magnitude fit is improved by moving the second pole of $G_p(s)$ further to the right, and the theoretical angle fit is improved by moving the same pole to the left; the pole location is chosen to satisfy both curves as much as possible, but it matches neither perfectly. This points to an unmodeled feature of the plant or compensator transfer function at high frequencies. Fortunately, near the gain crossover frequency, the theoretical and experimental data match quite well, which means that our compensator calculations are mostly valid for the region we designed them for.

The transfer function using the previous compensator values (from Lab 10) is plotted in orange. The new transfer function has a higher gain crossover frequency and a much healthier phase margin (68° vs. 42°), mostly due to the larger lead element phase boost. The angle also remains close to 90° for a much wider range of frequencies. One disadvantage of the new compensator is that the phase-crossover phase margin is smaller than before (-10dB vs. -17dB), because the magnitude drops off much later (greater bandwidth).

Closed-Loop Transfer Function (G)

```
In [ ]: w = closed loop bode["Frequency (Hz)"]
        G_{new} = G * Zc / (1 + G * Zc)
        GOL_gc = np.exp(1j * np.deg2rad(-180 + open_loop_gc_phase_margin))
        G_gc = GOL_gc / (1 + GOL_gc)
        print(f"Gain at cross-over frequency: {np.round(np.abs(G_gc), 3)} * exp({np.round(np.abs(G_gc), 3)} * exp({np.round(np.abs(G_gc), 3)})
        print(f"That's {np.round(to_decibels(np.abs(G_gc)), 2)} dB and {np.round(np.angle(G
        # zeta = 0.7
        zeta = 0.7
        w_gc = 14e3 * 2 * np.pi # open_loop_gc_freq * 2 * np.pi
        G_damping = w_gc ** 2 / ((2 * np.pi * 1j * w) ** 2 + 2 * zeta * w_gc * 2 * np.pi *
        print(f"Damping ratio used: {zeta}")
        print(f"Maximum gain of damped equation: {np.round(max(np.abs(G_damping)), 3)}")
        fig, (ax1, ax2) = plt.subplots(nrows = 2, ncols = 1, sharex = False, sharey = False
        helper.axes_labels("", "Hz", "Gain (dB)", "dB", title = "Bode Plot for Closed Loop
        ax1.semilogx(closed_loop_bode["Frequency (Hz)"], closed_loop_bode["Channel 2 Magnit
        ax1.semilogx(closed_loop_lab10["Frequency (Hz)"], closed_loop_lab10["Channel 2 Magn
        ax1.semilogx(closed_loop_bode["Frequency (Hz)"], to_decibels(G_new), linestyle = "d
        ax1.semilogx(w, to_decibels(G_damping), linestyle = "dashed", color = "purple", lab
        # ax1.axhline(y = to_decibels(np.abs(G_gc)), linestyle = "dashed", color = "black",
        # ax1.axvline(x = open_loop_gc_freq, linestyle = "dashed", color = "grey", label =
        ax1.legend(loc = "lower left")
        helper.axes_labels("Frequency (Hz)", "Hz", "Angle (degrees)", "o", title = "Bode Pl
        ax2.semilogx(closed_loop_bode["Frequency (Hz)"], np.unwrap(closed_loop_bode["Channe
        ax2.semilogx(closed_loop_lab10["Frequency (Hz)"], np.unwrap(closed_loop_lab10["Chan
        ax2.semilogx(closed_loop_bode["Frequency (Hz)"], np.unwrap(np.angle(G_new, deg = Tr
        ax2.axvline(x = open_loop_gc_freq, linestyle = "dashed", color = "grey", label = f"
        ax2.semilogx(w, np.unwrap(np.angle(G_damping, deg = True), period = 360), linestyle
        # ax2.axhline(y = -90, linestyle = "dashed", color = "black")
        ax2.legend(loc = "lower left")
        Gain at cross-over frequency: 0.885 * exp(-0.97j)
        That's -1.07 dB and -55.58 degrees
        Damping ratio used: 0.7
        Maximum gain of damped equation: 1.0
Out[ ]: <matplotlib.legend.Legend at 0x190dfac20a0>
```

 

This bode plot was taken on the upstream (closer to Vout) side of the feedback loop with reference to the *source* of the perturbation. The feedback loop is left intact and not accounted for separately, so this bode plot represents the response of the **closed-loop system** to a perterbation on the feedback line corresponding to a change in Vout.

The transfer function for a system with a damped second-order pole is given by $G(s) = \frac{\omega_0^2}{s^2 + 2\zeta\omega_0 s + \omega_0^2}, \text{ where } \omega_0 \text{ is the location of the pole. I asssumed that the pole would be located at the gain crossover frequency } \omega_0 = \omega_{gc}, \text{ but this produces a curve that is shifted too far to the left. I adjusted } \omega_0 \text{ and } \zeta \text{ until it matched the experimental data. The best fit was achieved with } \omega_0 = 14kHz \text{ and } \zeta = 0.7, \text{ although this method is not very sensitive to } \zeta. \text{ Again, the fit for the magnitude is better achieved when } \omega_0 \text{ is further to the right, whereas the fit for the angle is better when } \omega_0 \text{ is further to the left. I do not know how to explain this behavior.}$

The new compensator produces much better damping than the old design. The new compensator has a much higher bandwidth (higher even than expected based on G_p and Z_c). This might mean that the system is slightly less stable, because there is less attenuation of

signals near the switching frequency. This also leads to the smaller phase-crossover gain margin observed earlier.

```
In [ ]: df_step_response = pd.read_csv("bode_plots/lab11-step.csv")
        lab10_step_response = pd.read_csv("lab10_bode_plots/lab10_step_response_trace.csv")
        # print(df_step_response.head(5))
        def moving_average(x, w):
            w = int(w / 2) * 2
            convolution = np.convolve(x, np.ones(w), 'full') / w
            return convolution[int(w/2):-int(w/2)+1]
        df_step_response["Channel 1 (V)"] = -df_step_response["Channel 1 (V)"]
        df_step_response["Channel 2 (V)"] = -df_step_response["Channel 2 (V)"]
        # df_step_response["Ch2_moving_average"] = moving_average(df_step_response["Channel
        peak_idx = find_peaks(df_step_response["Channel 2 (V)"])[0]
        trough_idx = find_peaks(-df_step_response["Channel 2 (V)"])[0]
        df_peak_trace = df_step_response.copy().iloc[np.sort(np.concatenate((peak_idx, trou
        df_peak_trace["peak_moving_average"] = np.convolve(df_peak_trace["Channel 2 (V)"],
        df_step_response["Ch2_moving_average"] = moving_average(np.interp(df_step_response[
        df_zoom = df_step_response[(df_step_response["Time (s)"] > -1.1e-3) & (df_step_resp
        lab10_zoom = lab10_step_response[(lab10_step_response["Time (s)"] > -1.1e-3) & (lab
        # df_peak_trace_zoom = df_peak_trace_2[(df_peak_trace_2["Time (s)"] > -1.1e-3) & (d
        overshoot = np.max(df_zoom["Ch2_moving_average"]) # 10.6 # V
        top_steady_state = overshoot - 0.05 # = 10 # V
        undershoot = np.min(df_zoom["Ch2_moving_average"]) # 8.5 # V
        bottom_steady_state = undershoot + 0.04 # = 9.13 # V
        output_swing = top_steady_state - bottom_steady_state
        overshoot_ratio = (overshoot - top_steady_state) / output_swing
        zeta_from_overshoot = np.sqrt(np.log(overshoot_ratio) ** 2 / (np.pi ** 2 + np.log(o
        print(f"Output swing: {si_format(output_swing, precision = 2)}V for a 1V perturbati
        print(f"That's a gain of {np.round(output_swing / 1.0, 2)}")
        print(f"It overshoots by {si_format(overshoot - top_steady_state, precision = 2)}V
        print(f"Zeta from overshoot: {np.round(zeta_from_overshoot, 2)}")
        print(f"Zeta from earlier (for comparison): {np.round(zeta, 2)}")
        fig, (ax1_left) = plt.subplots(nrows = 1, ncols = 1, sharex = False, sharey = True,
        ax1_right = ax1_left.twinx()
        fig.autofmt_xdate()
        helper.axes_labels("Analog Discovery timestamp", "s", "Channel 1 (perturbation)", "
        helper.axes_labels("Analog Discovery timestamp", "s", "Channel 2 (Vout)", "V", titl
        ax1_left.plot(df_zoom["Time (s)"], df_zoom["Channel 1 (V)"], color = "royalblue", 1
        ax1_right.plot(df_zoom["Time (s)"], df_zoom["Channel 2 (V)"], color = "orange", lab
        ax1_right.plot(df_zoom["Time (s)"], df_zoom["Ch2_moving_average"], color = "green",
        ax1_right.plot(lab10_zoom["Time (s)"], lab10_zoom["Ch2_moving_average"], color = "p
        # ax1_right.axhline(y = overshoot, linestyle = "dashed", color = "black", label = "
        # ax1_right.axhline(y = top_steady_state, linestyle = "dashed", color = "black", la
        # ax1_right.axhline(y = bottom_steady_state, linestyle = "dashed", color = "black",
        # ax1_right.axhline(y = undershoot, linestyle = "dashed", color = "black", label =
        ax1 left.yaxis.label.set color('royalblue')
```

```
ax1_left.tick_params(axis='y', colors='royalblue')
ax1_right.tick_params(axis='y', colors='darkorange')
ax1_right.yaxis.label.set_color('darkorange')
ax1_right.legend(loc = "lower right")
```

Output swing: 831.95 mV for a 1V perturbation


That's a gain of 0.83

It overshoots by 50.00 mV and undershoots by 40.00 mV

Zeta from overshoot: 0.67

Zeta from earlier (for comparison): 0.7

 Out[]: <matplotlib.legend.Legend at 0x190e467b5b0>



A 1V square-wave perturbation was applied to the feedback loop. The output voltage had time to settle between each cycle, so the response can be analyzed like a step response. The output voltage ripple (orange) is inherent to the power converter, so what we care about is the DC output voltage response (green). The output voltage is centered around 10.07V and swings by around 830mV in response to the 1V feedback perturbation. In my Lab 10 report, I mistakenly thought the perturbation was a 100mV step change, not 1V. I reported that there was a large gain between the perturbation and the output response, when in reality, there is slightly less than unity gain.

According to this resource, the damping ratio ζ can be obtained from the overshoot ratio $O=\frac{\text{overshoot}}{\text{output swing}}$ by the equation $\zeta=\sqrt{(\frac{ln^2(O)}{\pi^2+ln^2(O)})}$. Plugging in the values for overshoot and output swing yields a damping ratio of $\zeta=0.67$. This is very similar to the damping ratio of 0.7 found earlier.

Compared with the previous compensator, the new design yields an output voltage much closer to 10.0V (10.00V-10.07V vs. 9.60V), improved phase margin (68° vs. 42°), and greater damping ratio (0.67 vs. 0.45) which nearly eliminates the overshoot while still converging quickly. In conclusion, I believe that our compensator comonent values are very close to ideal.